



Daffodil International University  
Department of Electrical and Electronic Engineering  
Faculty of Engineering






**Final Examination, Fall – 2023 (Day)**






Course Code: 0713-121  
Section: A, B, C, D  
Full Marks: 25

Course Title: Electrical Circuits II  
Level-Term: L1-T2  
Exam Date: September 23, 2023

Teacher's Initial: MSA, KNN  
Time: 1.5 Hours

*Answer any five out of seven*

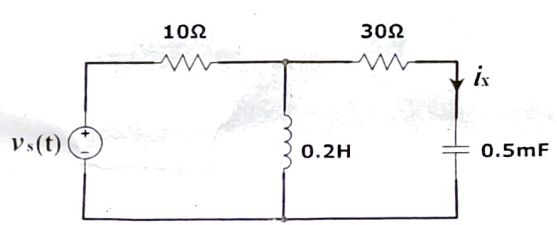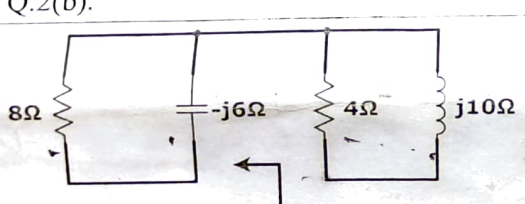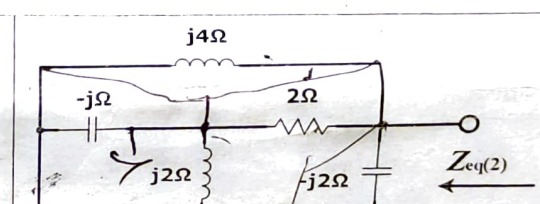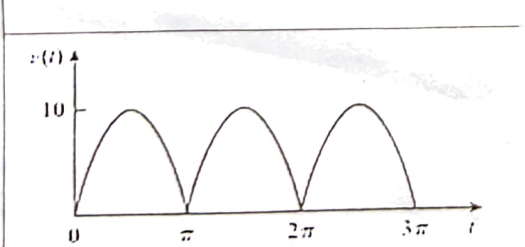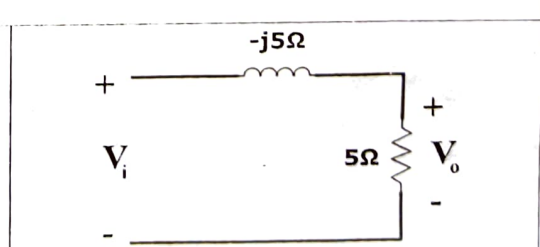Q.1	<p>If <math>v_s(t) = 20 \sin(100t - 40^\circ)</math> volt, find <math>i_x(t)</math> in the following figure Q.1.</p>  <p style="text-align: center;">Fig: Q.1</p>	CO-1 C(2) 5
Q.2	<p>Find the equivalent impedance <math>Z_{eq(1)}</math> in the following figure Q.2(a) &amp; <math>Z_{eq(2)}</math> in figure Q.2(b).</p> <div style="display: flex; justify-content: space-around;"><div data-bbox="207 1030 734 1299"><p style="text-align: center;">Fig: Q.2(a)</p></div><div data-bbox="734 1030 1276 1299"><p style="text-align: center;">Fig: Q.2(b)</p></div></div>	CO-1 C(2) 5
Q.3	<p>(a) Find the r.m.s. value of the full wave rectified voltage in figure Q.3(a). (b) Calculate the phase shift angle by the RL circuit in figure Q.3(b).</p> <div style="display: flex; justify-content: space-around;"><div data-bbox="207 1411 734 1747"><p style="text-align: center;">Fig: Q.3(a)</p></div><div data-bbox="734 1411 1276 1747"><p style="text-align: center;">Fig: Q.3(b)</p></div></div>	CO-2 C(2) 5

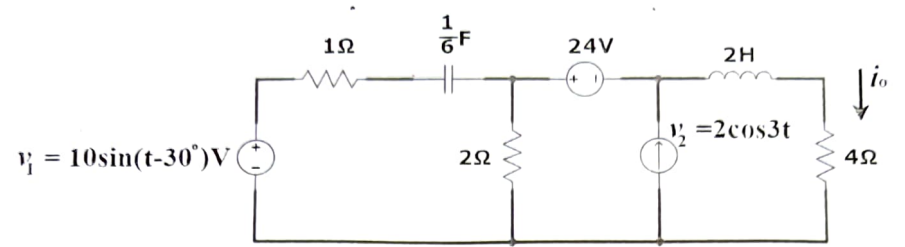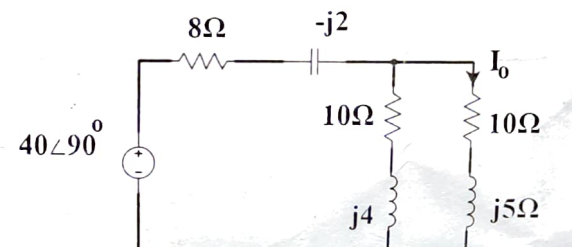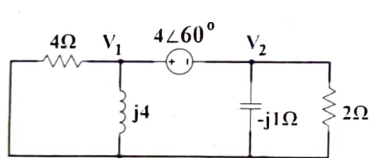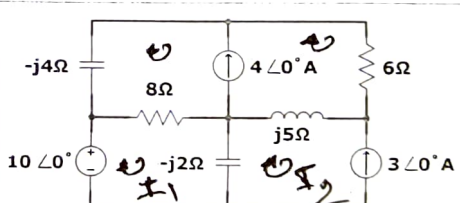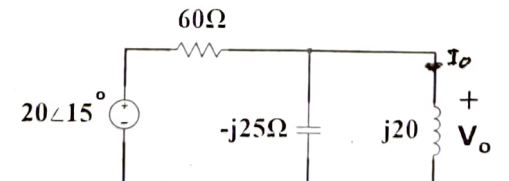Q.4	<p>(a) Determine <math>i_o</math> in the following figure Q.4, when DC voltage source is active only.</p> <p>(b) Calculate the reactances when (1) <math>v_1</math> is active only, and (2) <math>v_2</math> is active only</p>  <p style="text-align: center;">Fig: Q.4</p>	CO-2 C(3) 5
Q.5	<p>Calculate <math>I_o</math> in the following circuit using (a) Norton's theorem, and (b) Thevenin's theorem.</p>  <p style="text-align: center;">Fig: Q.5</p>	CO-2 C(3) 5
Q.6	<p>(a) Obtain the nodal equations for the following figure Q.6(a).</p> <p>(b) Obtain the equation for the super mesh in the following figure Q.6(b).</p> <div style="display: flex; justify-content: space-around;">   </div> <div style="display: flex; justify-content: space-around;"> <p style="text-align: center;">Fig: Q.6(a)</p> <p style="text-align: center;">Fig: Q.6(b)</p> </div>	
Q.7	<p>(a) Using current divider rule, calculate <math>I_o</math> in the following figure Q.7.</p> <p>(b) Using concept of source theorem, calculate also <math>I_o</math>.</p>  <p style="text-align: center;">Fig: Q.7</p>	