



Daffodil International University

Faculty of Science & Information Technology

Department of Computer Science & Engineering

Midterm Examination, Fall 2025

Course Code: CSE 121 , Course Title: Electrical Circuits



Level:1 Term:3 Batch: 68



Time: 01:30 Hrs

Marks: 25

Answer ALL Questions [Optional]

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

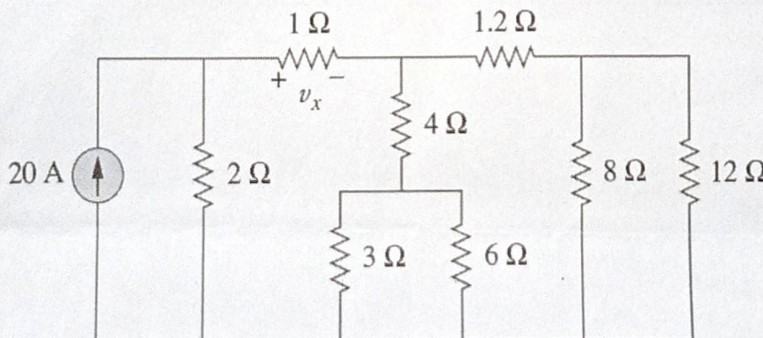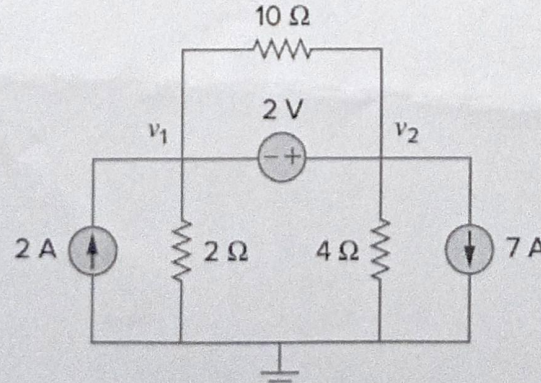
1.	<p>a) What is node and branch?</p> <p>b) If the length of a conductor is doubled and its radius is reduced to half of its original value, what will be its new resistance?</p> <p>c) Define open and short circuit.</p> <p>d) How does temperature affect conductors and semiconductors?</p> <p>e) Explain the concept of a supernode in circuit analysis.</p>	5×1=5	CO1
2.	<p>a) Solve the following circuit to determine v_x and the power absorbed by the 2Ω resistor.</p> 	5	CO2
	<p>b) Solve the following circuit using nodal analysis to identify node voltages.</p> 	5	

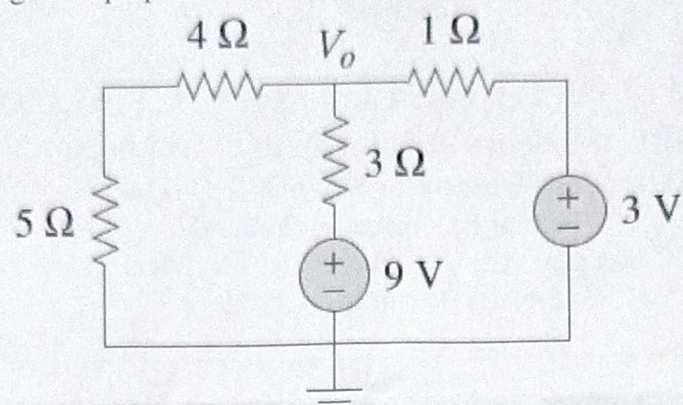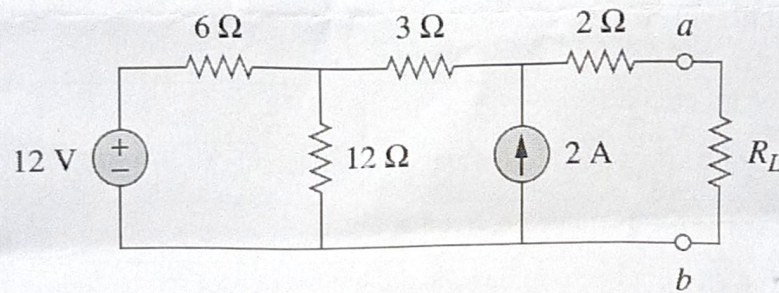3. a)	<p>Examine the following circuit to determine the current through the $3\ \Omega$ resistor using the superposition theorem.</p> 	5	CO3
b)	<p>Analyze the following circuits to-</p> <ol style="list-style-type: none"> Determine the Thevenin equivalent resistance at terminals a-b. Find R_L for maximum power deliverable to R_L. Determine that maximum power. 	5	


Solved by:
Md. Abdullah Al Fahim
251-15-210
Department of Computer Science and Engineering (DIU)

Answer: 2(a)

Give Circuit:

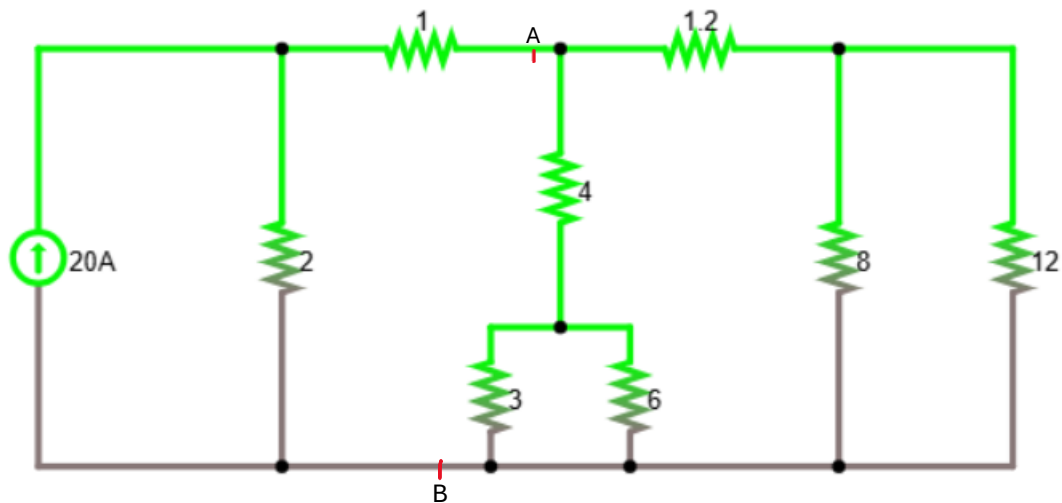

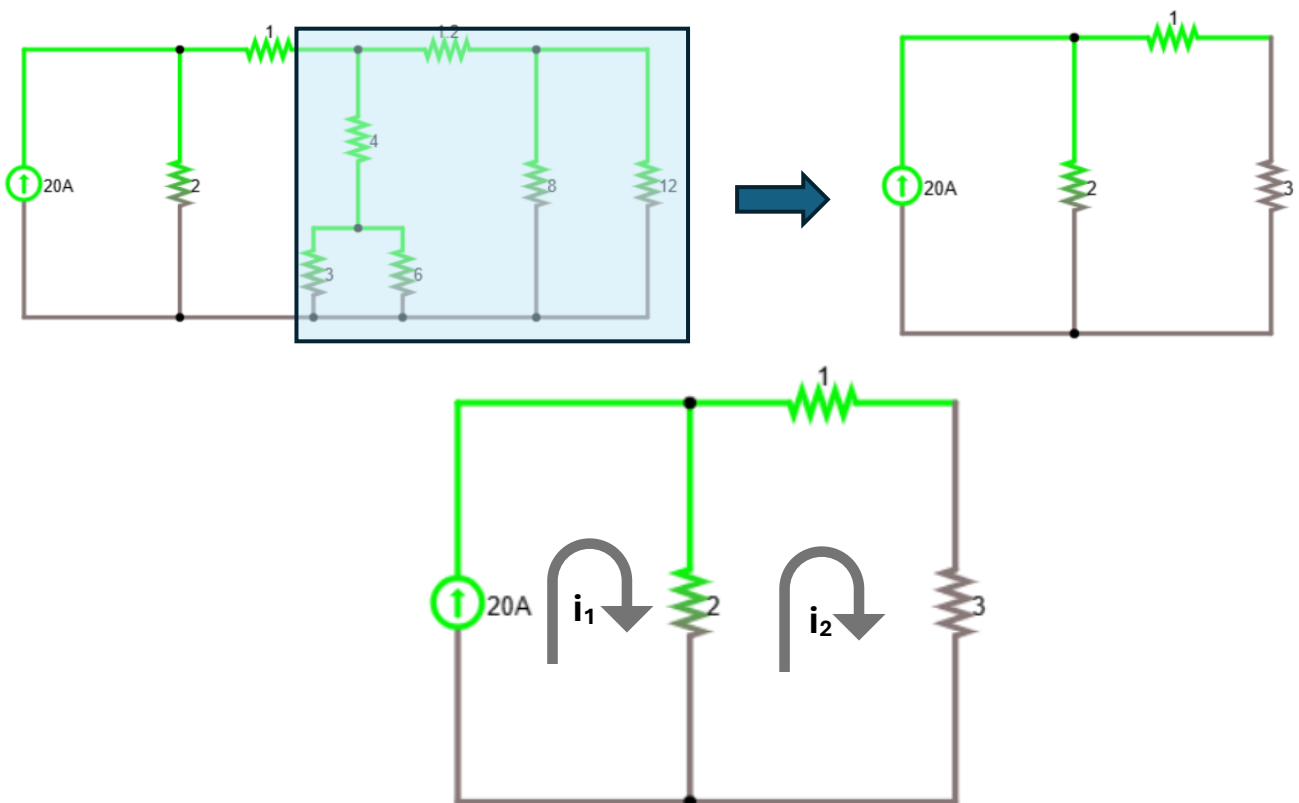Calculate equivalent resistance of the right portion of A and B.



From the circuit we get:

$$i_1 = 20\text{A}$$

Applying KVL at node-2:

$$2(i_2 - 20) + i_2 + 3i_2 = 0$$

$$\Rightarrow i_2 = 6.67\text{A}$$

So, Voltage through 1Ohm resistor

$$V_0 = i_2 R = 6.67 \times 1 = 6.67\text{V}$$

Again, Current through 2Ohm resistor


$$I_{R2} = i_1 - i_2 = 20 - 6.67 = 13.33\text{A}$$

So, Power Absorbed by 2Ohm resistor ,

$$P = (I_{R2})^2 R = (13.33)^2 \times 2 = 355.56\text{W}$$

Answer: 2(b)

Given Circuit:

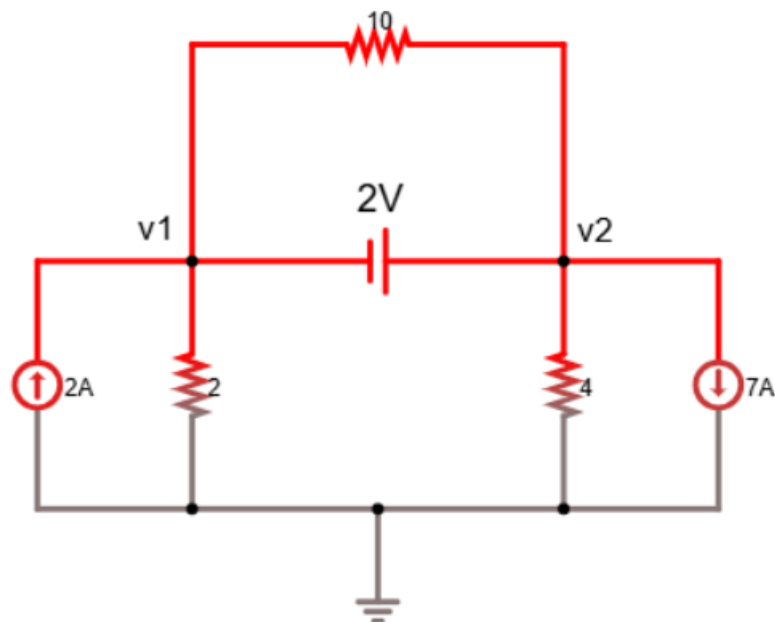

There is a voltage source between node-1 and node-2. So, node-1 and node-2 forms a Supernode.

Applying KCL at supernode:

$$-2 + \frac{v_1}{2} + \frac{v_1 - v_2}{10} + \frac{v_2 - v_1}{10} + \frac{v_2}{4} + 7 = 0$$

$$\Rightarrow 2v_1 + v_2 = -20 \text{ -----(i)}$$

Supernode equation:


$$v_2 - v_1 = 2$$

$$\Rightarrow v_1 - v_2 = -2 \text{ -----(ii)}$$

By solving equations:
 $v_1 = -7.33 \text{ v}$
 $v_2 = -5.33 \text{ v}$

Answer: 3(a)

Given Circuit:

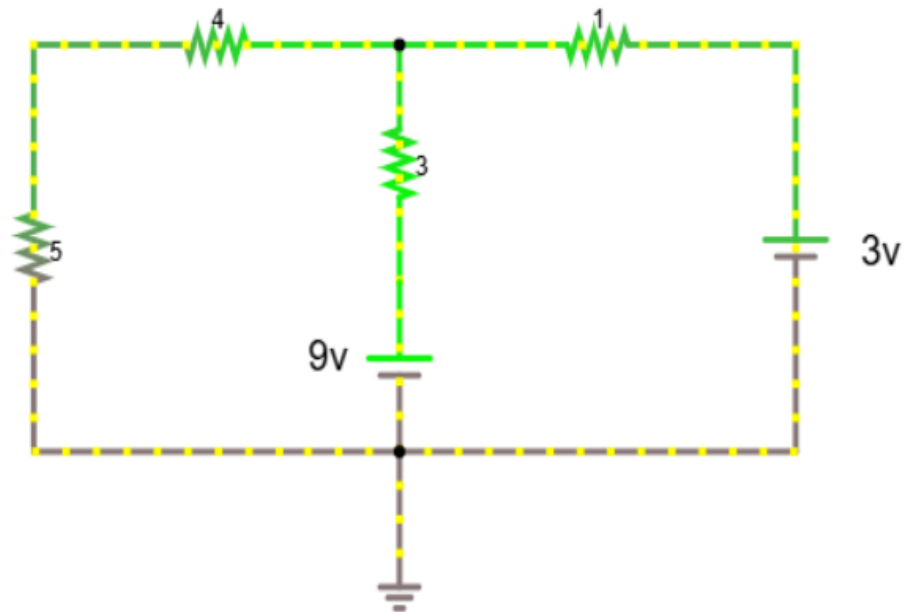

For 9v voltage source current through the 3Ohm resistor:

Applying KVL to loop-1:

$$5i_1 + 4i_1 + 3(i_1 - i_2) + 9 = 0$$

$$\Rightarrow 12i_1 - 2i_2 = -9 \text{ -----(1)}$$

Applying KVL to loop-2:

$$3(i_2 - i_1) + i_2 - 9 = 0$$

$$\Rightarrow -3i_1 + 4i_2 = 9 \text{ -----(2)}$$

Solving two equations:


$$i_1 = -0.231$$

$$i_2 = 2.076$$

Current through 3Ohm resistor

$$I_{9v} = i_2 - i_1 = 2.076 - (-0.231)$$

$$= 2.307 \text{ A}$$

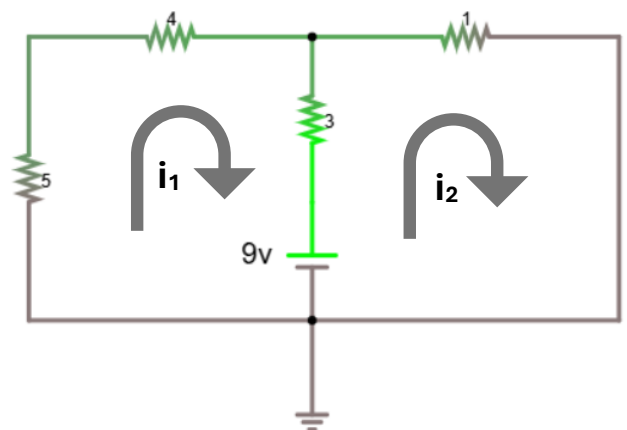

For 3V voltage source current through 3Ohm resistor:

Applying KVL to loop-1:

$$3i_1 + 4i_1 + 3(i_1 - i_2) = 0$$

$$\Rightarrow 12i_1 - 3i_2 = 0 \quad \text{-----(i)}$$

Applying KVL to loop-2:


$$3(i_2 - i_1) + i_2 + 3 = 0$$

$$\Rightarrow 3i_1 - 4i_2 = 3 \quad \text{-----(ii)}$$

By solving equations:

$$i_1 = -0.231$$

$$i_2 = -0.923$$

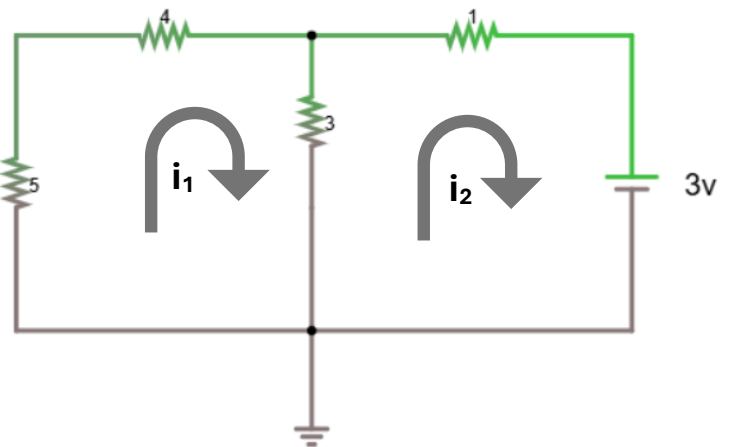

Current through 3Ohm resistor for 3V voltage source

$$I_{3V} = i_2 - i_1 = -0.923 - (-0.231)$$

$$= -0.692 \text{ A}$$


Total current through 3Ohm resistor:

$$I = I_{9V} + I_{3V} = 2.307 + (-0.692) \text{ A}$$

$$= 1.615 \text{ A}$$

Answer 3(b)

Given Circuit

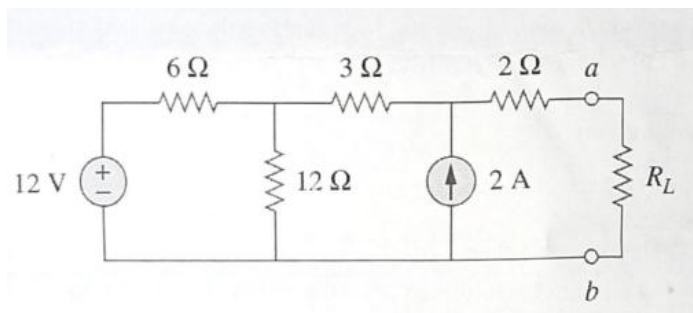


i) Detach the Current and voltage sources to calculate Thevenin equivalent resistance:

$$R_{Th} = (6 \parallel 12) + 3 + 2 \text{ Ohm}$$

$$= 9 \text{ Ohm}$$

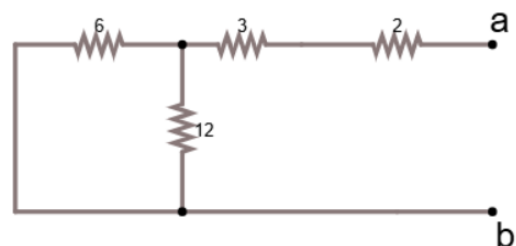ii) The **Maximum Power Transfer Theorem** states that the maximum power is delivered to a load resistor R_L when R_L is equal to the




Thevenin equivalent resistance R_{Th} of the source network as seen from the load terminals.

$$R_L = R_{Th} = 9\Omega$$

iii)

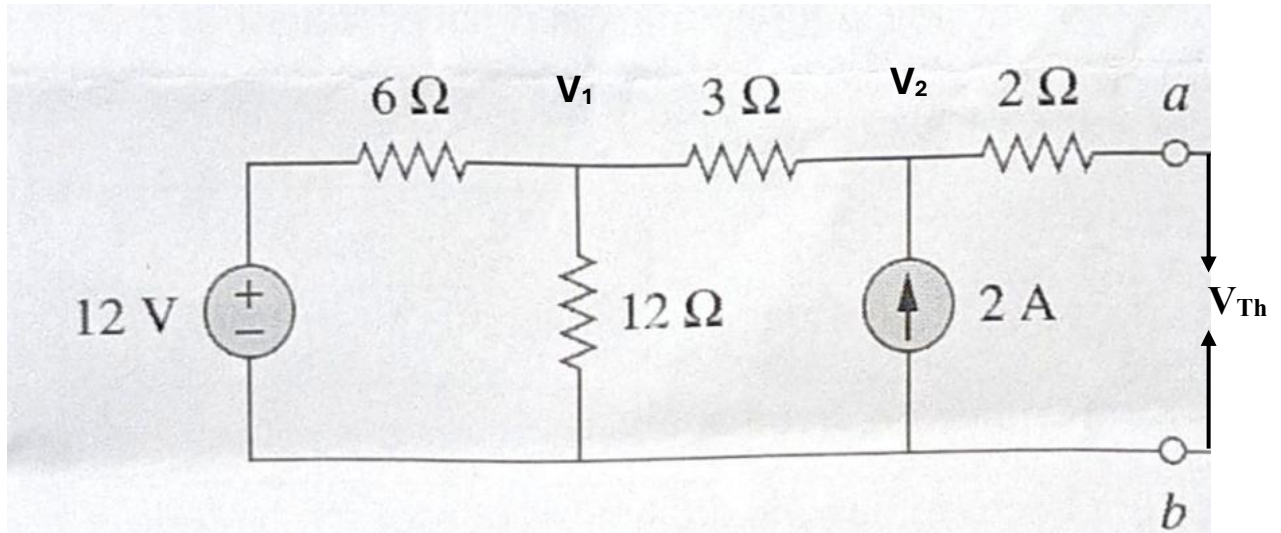[**Note:** This solution contains possible inaccuracies. Kindly cross-check and confirm.]



Applying KCL to Node-1:

$$\frac{v1 - 12}{6} + \frac{v1 - v2}{3} + \frac{v1}{12} = 0$$

$$\Rightarrow 7V_1 - 4V_2 = 24 \text{ -----(1)}$$

Applying KCL to Node-2:

$$\frac{V_2 - V_1}{3} - 2 = 0$$

$$\Rightarrow -V_1 + V_2 = 6 \text{ -----(2)}$$

By solving equations, we get

$$V_1 = 16$$

$$V_2 = 22$$

So, $V_{Th} = V_2 = 22V$

Maximum Power,

$$P_{Max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{22^2}{4 \times 9} = 13.44W$$