



Daffodil International University

Faculty of Science & Information Technology

Department of Computer Science & Engineering

Mid Semester Examination, Fall-2024

Course Code: CSE223, Course Title: Digital Logic Design


Level: 2 Term: 2 Batch: 64

Time: 1.5 Hrs

Marks: 25

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

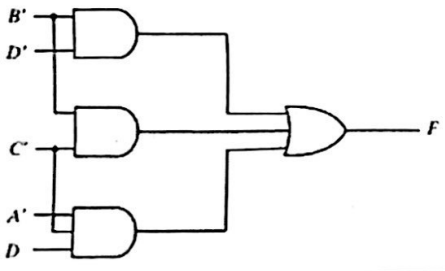1.	a)	Show the types of digital number system and show the conversion of following numbers: 1. $(85203.416)_9 = (?)_7$ 2. $(42673.271)_{10} = (?)_4$	4	CO1
	b)	Demonstrate the following Boolean function using only NOR gates $F(A,B,C,D) = (AB'C) + (A'D) + (BC')$	4	
2.	a)	Construct a simplified expression of the following Boolean expression using simplification law. $F(A,B,C) = (ABC') + (A'(B+C)(B'+C'))(A+BC)$	4	CO2
2	b)	Illustrate the Boolean expression of the following circuit and develop its standard form using sum of minterms (SOP). 	4	
	c)	Apply the simplification of the following Boolean function using K-map with sum of minterm: $F(A,B,C,D) = \Sigma(0, 1, 3, 4, 5, 12, 15) + \Sigma d(2, 3, 10, 11)$	4	
3.	a)	You are assigned to develop a fire alarm system in a building that operates based on the following sensors: <ul style="list-style-type: none"> S: 1 if smoke is detected, 0 otherwise. T: 1 if high temperature is detected, 0 otherwise. M: 1 if the manual alarm is activated, 0 otherwise. The fire alarm (F) should be activated under these conditions: 1. $F=1$ when smoke is detected and high temperature is detected. 2. $F=1$ when smoke is detected and the manual alarm is activated. 3. $F=1$ when high temperature is detected or the manual alarm is activated. Now, Construct the truth table for F, derive the Boolean expression and draw the logic circuit diagram.	5	CO3