



**Daffodil International University**  
Department of Electrical and Electronic Engineering  
Faculty of Engineering  
**Mid-Term Examination, Spring – 2025**

Course Code: 0713-213

Section: A / B / C

Full Marks: 25

Course Title: Energy Conversion I

Level-Term: L2-T1

Exam Date: March 11, 2025

Teacher's Initial: DRA

Time: 1.5 Hours

**Attempt to Answer all 4 Questions**

- Q1. a) Derive the EMF equation of a single-phase transformer.** **CO-1 3**  
**C(3)**
- b) A 25 kVA, 230/11000 V single-phase, 50 Hz transformer has 2400 turns in its high voltage side winding.** **CO-1 4**  
**C(3)**  
**Calculate** (i) full-load primary and secondary currents, (ii) the number of turns in its low-voltage side and (iii) the maximum flux in the iron core.
- Q2. a) Describe with supporting figures that whatever the load conditions, the net flux passing through the core is approximately the same as at no-load.** **CO-1 3**  
**C(2)**
- b) A single-phase transformer has 75 turns in secondary and 320 turns in primary. The no-load power factor is 0.1736 lagging and the magnetizing component of no-load primary current is 4.7 A. If the load component of primary current ( $I_2'$ ) is 35 A at 0.891 lagging. Determine the no-load current ( $I_0$ ) and the current delivered by secondary ( $I_2$ ).** **CO-1 4**  
**C(3)**
- Q3. a) Explain - how the exciting circuit components are measured using open-circuit test of a transformer. Provide free-hand drawing and associated equations.** **CO-2 2**  
**C(2)**
- b) A 20 kVA, 2200/240 V, 50 Hz transformer has a high-voltage winding resistance of 0.15  $\Omega$  and a leakage reactance of 0.35  $\Omega$ . The low-voltage winding has a resistance of 0.04  $\Omega$  and a leakage reactance of 0.015  $\Omega$ .** **CO-2 4**  
**C(5)**  
**Find** the equivalent winding resistance, reactance and impedance referred to the (i) high-voltage side and (ii) the low-voltage side and (iii) total  $Cu$  loss of the transformer.
- Q4. A 25 kVA, 2300/240 V, 50 Hz transformer has  $R_1=25 \Omega$ ,  $X_1=110 \Omega$ ,  $R_2=0.05 \Omega$ ,  $X_2=0.4$ , no-load current of 4.5 A leading the flux by  $25^\circ$  and delivers full-load secondary current of 130 A at 240 V with a power factor of 0.85 lagging.** **CO-2 5**  
**C(5)**  
**Calculate the supply voltage.**