



Daffodil International University
Department of Software Engineering
Faculty of Science & Information Technology
Final Examination, Fall 2023

Course Code: SE 213; Course Title: Digital Electronics & Logic design
Batch: 40; Sections: All

Time: 2:00 Hrs

Marks: 40

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

1	a) Apply k-map simplification technique to simplify the following function. Construct the logic diagrams of the simplified output. $F(m,n,o,p) = \sum (0,2,4,5,6,7,12,13,14,15)$	[Marks-5] #4 m-n-p	CLO-2 Level-3
	b) Design a full adder by obtaining the simplified expressions for the sum And carry outputs using basic logic gates.	[Marks-5]	
2	a) Develop 4 to 16 decoder using 3 to 8 decoder.	[Marks-5]	CLO-3 Level-3
	b) Utilize the concept of an Encoder circuit to build Octal to binary converter.	[Marks-5]	
	c) Build the following function using Multiplexer. $F(A,B,C,D) = \sum (1,2,4,7,10,12,13,14,15)$	[Marks-5]	
	d) Design an 8X1 Demultiplexer following necessary steps.	[Marks-5]	
3	a) Explain the working principle of Serial Input serial Output (SISO) Shift register.	[Marks-5]	CLO-4 Level-5
	b) "JK flip flop is used to remove the drawback of the S-R flip flop". Justify the above statement with appropriate circuit diagram.	[Marks-5]	